

Lab 4. Combinational Logic Design

- 1) Build a non-prime-number detector circuit. (100 pts)
 - a. First, complete the truth table below. If the integer $A_3A_2A_1A_0$ is a prime number, the output O should be 0. Otherwise, O should be 1. Note that 1 is not a prime number.
 - b. Use a K-map to optimize the function O.
 - c. Build a circuit in Vivado and show results on simulation part.
- 2) Files to submit;
 - A. K-map picture (you can take your notebook picture)
 - B. Block design picture
 - C. Simulation result picture. In this part show each 16 possibilities for input combinations with an order which is given in truth table.

Table 1. Truth table.

A_3	A_2	A_1	A_0	O
0	0	0	0	1
0	0	0	1	1
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	