

### Assignment

Design and simulate the circuit given below.

Try all input combinations in your simulation. Input order must be in the table below.

A	B
0	0
0	1
1	0
1	1

Submit;

1. Block Design picture (not elaborated design)
2. Simulation result picture

